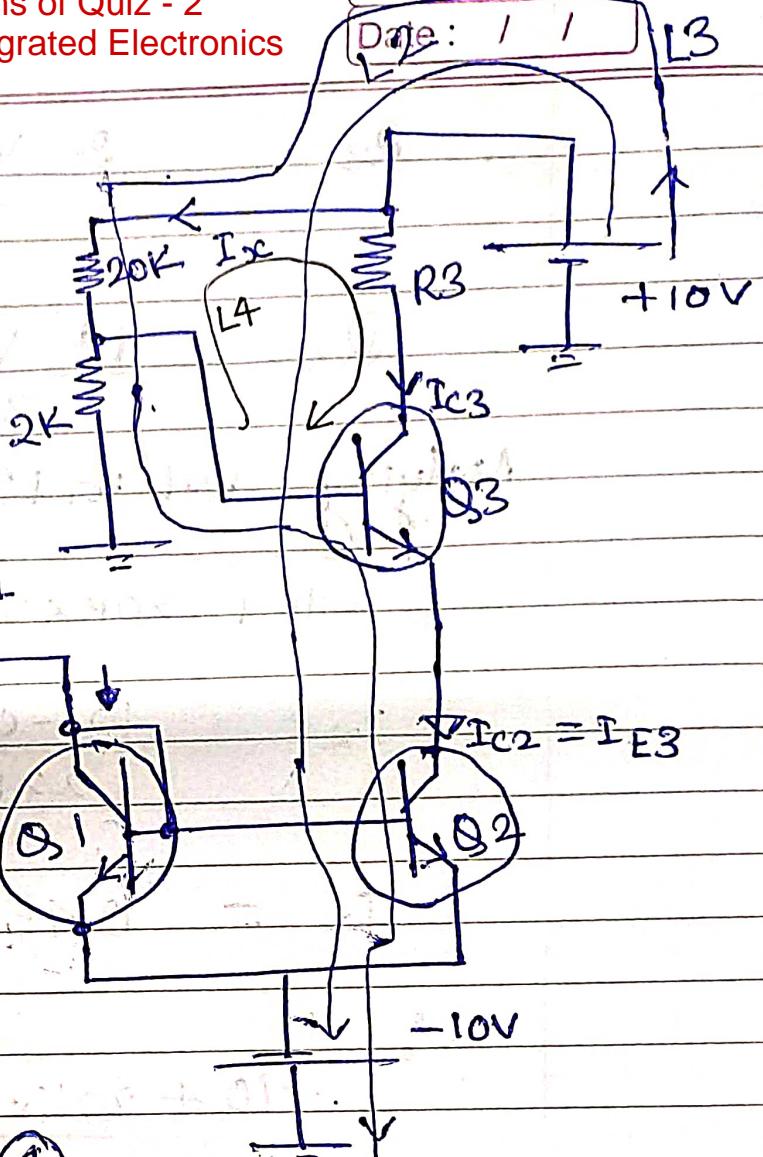


Q1 > Q3

For Q3 we have to

$$\text{set } I_{C3} = 3 \text{ mA}$$

$$V_{CE3} = 6 \text{ V}$$



Applying KVL on L1

$$-R_4 I_4 - 0.7$$

$$-V_{BE1} + 10 = 0$$

$$\therefore R_4 = \frac{10 - 0.7 - 0.7}{I_4}$$

$$R_4 = \frac{10 - 1.4}{I_4} = \frac{8.6}{I_4}$$

Since Q1 and Q2 are perfectly matched and they are forming a Current mirror

$$\therefore I_{C1} = I_{C2}$$

Neglecting base current

$$I_4 \approx I_{C1} = I_{C2} = I_{E2} \approx I_{C3} = 3 \text{ mA}$$

$$\therefore R_4 = \frac{8.6}{3 \text{ mA}} \approx 2.87 \text{ k}\Omega$$

Now, Applying KVL on L2

$$-10 + 3 \text{ mA} \times R_3 + V_{CE3} + V_{EE2} - 10 = 0$$

$$\therefore R_3 = \frac{20 - V_{CE3} - V_{CE2}}{3 \text{ mA}} = \frac{20 - 6 - V_{CE2}}{3 \text{ mA}}$$

$$\therefore R_3 = \frac{14 - V_{CE2}}{3 \text{ mA}} \quad \textcircled{2}$$

Applying KVL on L3

$$-10 + 20K \times I_x + 0.7 + V_{CE2} - 10 = 0$$

$$I_x = \frac{10 - 0}{22K} \quad (\text{Neglecting base currents})$$

$$I_x = 0.45 \text{ mA}$$

$$\therefore -10 + 20K \times 0.45 \text{ mA} + 0.7 + V_{CE2} - 10 = 0$$

$$\therefore V_{CE2} = \frac{20 - 9.09 - 0.7}{1} = 10.21 \text{ V}$$

$$\therefore V_{CE2} = 10.21 \text{ V} \quad \textcircled{3}$$

by $\textcircled{2}$ & $\textcircled{3}$

$$R_3 = \frac{14 - 10.21}{3 \text{ mA}} = 1.26 \text{ kV}$$

$$\therefore R_4 = 2.87 \text{ kV}$$

$$\& R_3 = 1.26 \text{ kV}$$

Ane

Q.1.(b) for Q3 to remain in active region

$$V_{CE3} > 0.2V$$

From L2

$$-10 + I_{C3}R_3 + V_{CE3} + 10 \cdot 21 - 10 = 0$$

$$\therefore I_{C3}R_3 + V_{CE3} = 20 - 10 \cdot 21$$

From L1

$$I_4 = \frac{10 - 1.4}{R_4}$$

$$\therefore I_4 = I_{C3}$$

$$\therefore \frac{8.6}{R_4} \cdot R_3 + V_{CE3} = 9.79 \quad \text{--- (1)}$$

Hence, $V_{CE3} = 9.79 - 8.6 \frac{R_3}{R_4}$

i. For Q_3 to remain in active region

$$9.79 - 8.6 \frac{R_3}{R_4} > 0.2$$

$$\frac{R_3}{R_4} < \frac{9.79 - 0.2}{8.6}$$

$\therefore \boxed{\frac{R_3}{R_4} < 1.12}$

Here, we see that at a particular R_4

Q_3 collector current will be biased according to the current mirror, which will be independent of R_3 .

However, as per Q_3 , V_{CE3} will change.

\therefore Range of R_4 will be

$\boxed{R_4 \rightarrow \frac{R_3}{1.12}}$


Q. 2: (a)

$$I_D = 0.1 \text{ mA}$$

$$0.1 = \frac{1}{2} I_m C_o x (W/L) (V_{DS} - V_T)^2$$

$$V_{DS} - V_T = 0.1 \text{ m}$$
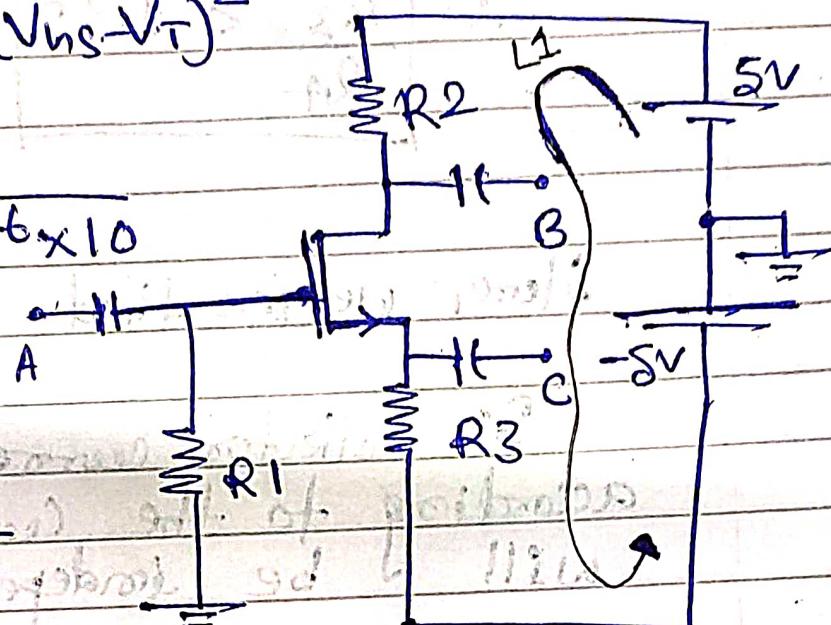
$$\frac{1}{2} \times 80 \times 10^{-6} \times 10$$



$$V_{DS} - V_T = \frac{10(4+4)}{2A} = 4 \text{ m}$$

$$\therefore V_{DS} - V_T = 0.25 \text{ m}$$

$$\therefore V_{DS} = 0.25 + V_T = 1.25 \text{ V}$$

$$V_{in} - V_S = 1.25$$

$$\therefore V_S = V_h - 1.25 = 0 - 1.25 = -1.25$$

~~$$\therefore V_S = 0.1 \text{ mA}$$~~


$$\therefore \frac{5 - 1.25}{R_3} = 0.1$$

$$R_3 = \frac{4.75}{0.1} = 47.5 \text{ k}\Omega$$

Applying KVL on L1

$$2(0.1R_2 + V_{DS}) - 5 = 0$$
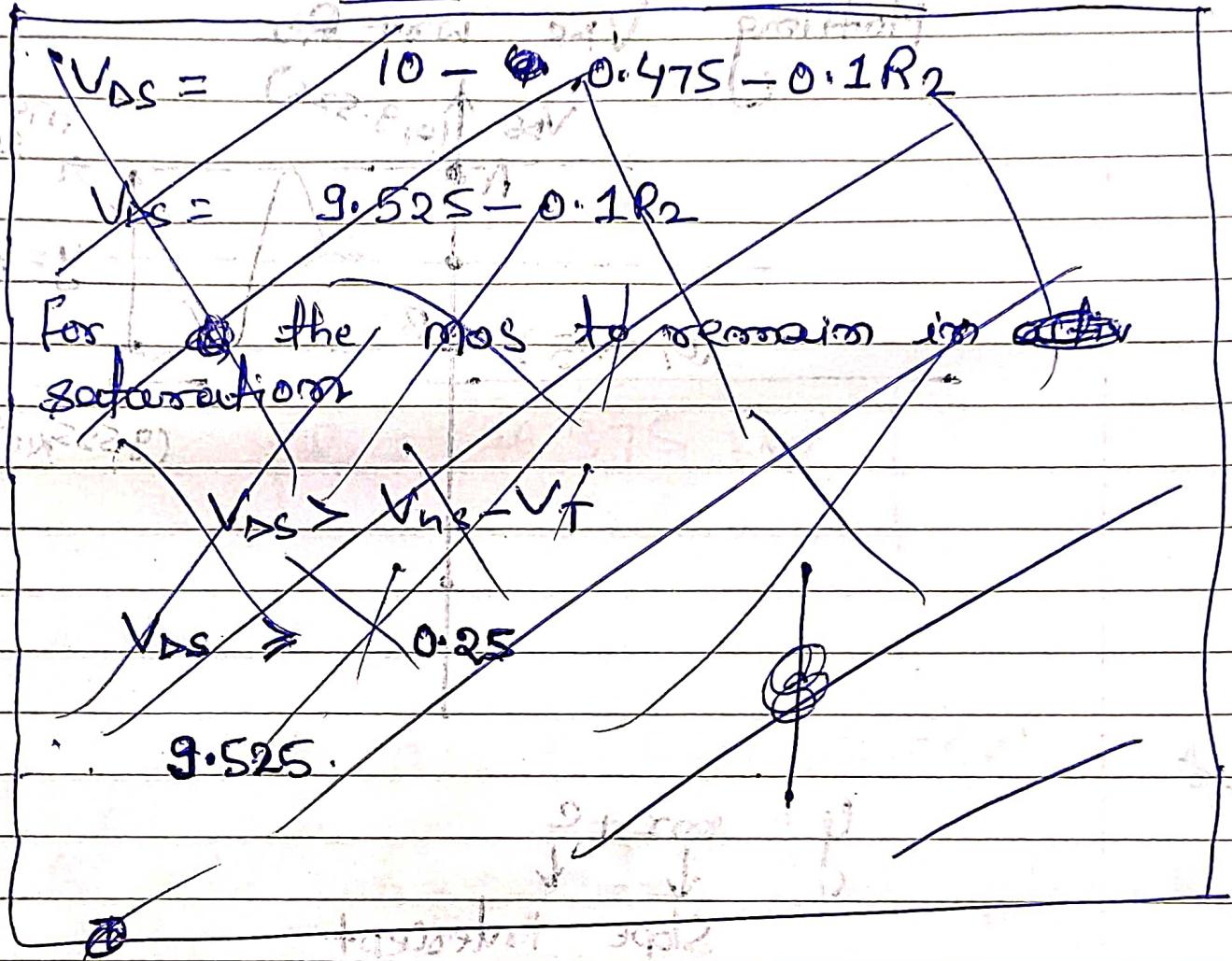
$$-5 + 0.1R_2 + V_{DS} + 4.75 \times 0.1 - 5 = 0$$



$$-5 + I_D R_2 + V_{DS} + 4.75 I_D - 5 = 0$$

$$I_D (R_2 + 4.75) + V_{DS} = 10$$

$$0.1 m R_2 + 4.75 \times 0.1 m + V_{DS} = 10$$


$$0.1 m R_2 + V_{DS} = 10 - 0.475 = 9.525$$

$$0.1 \times 10^{-3} R_2 + V_{DS} = 9.525$$

08

$$V_{DS} = -10^{-4}R_2 + 9.525$$

Plotting V vs $\log R_2$

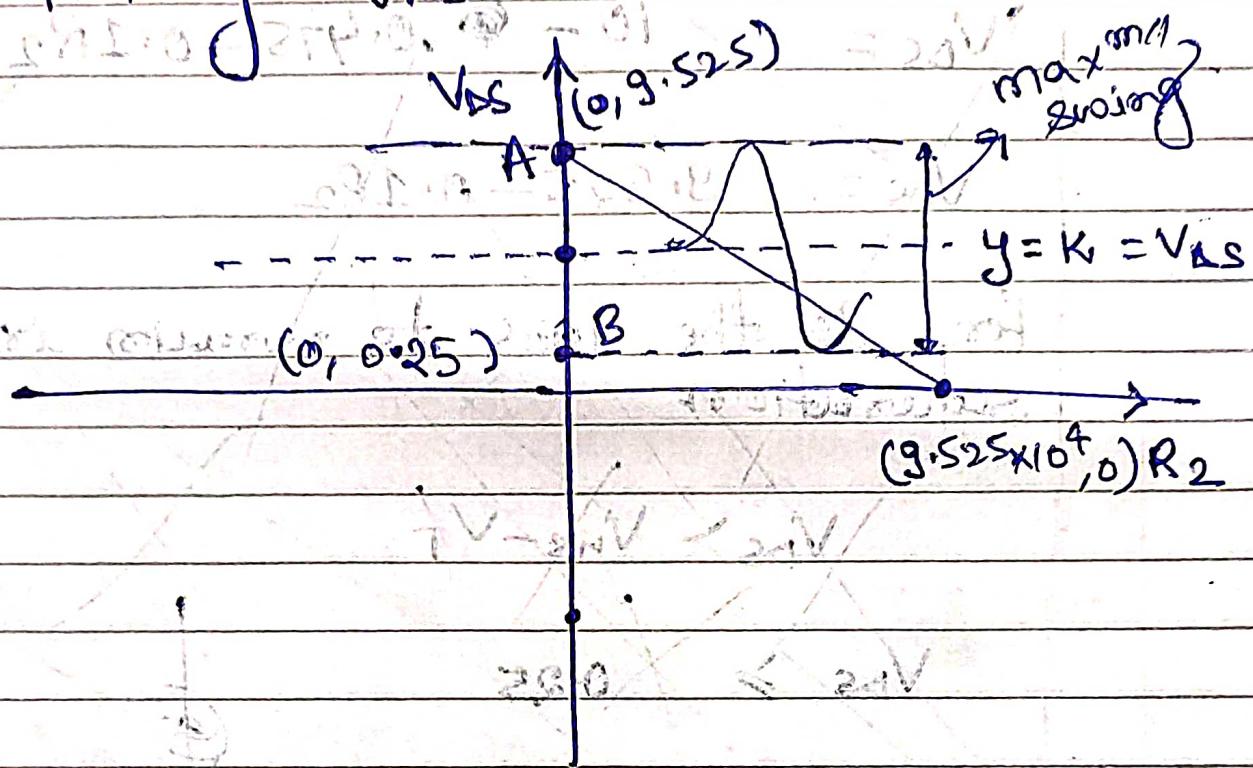

$$y = mx + c$$

$\downarrow \quad \downarrow$

Slope intercept

Since, for the MOSFET remain in saturation mode

$$H = \omega N + (25.44\text{eV})qT$$

$V_{DS} > V_{DS-VI} > 0.25$

for a maximum possible swing out, $I \geq 0.1 \text{ mm}^4$, the respective R_2 should come over the mid-point of A and B.

$$\therefore K = \frac{9.525 + 0.25}{2} \approx 4.887$$

$$\therefore R_2 = \frac{9.525 - 4.887}{10^4}$$

~~$R_2 \approx 4.61 \times 10^4$~~

~~$R_2 = 46.35$~~


$$R_2 = 46.375 \text{ kN}$$

Q. 2 b) Given that

$$I_D = 0.1 \text{ mA}, R_2 = 46.375 \text{ kN}$$

If node C is grounded, C₃ will bypass R₃ for AC signals.

Hence drawing the small signal model.

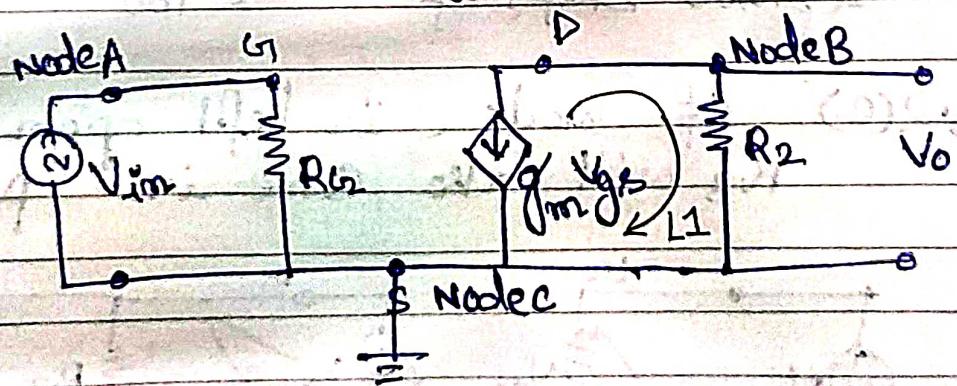

~~$V_{gs} = V_{im}$~~

$$\text{For } L_1 \text{ } \therefore V_o = -g_m V_{gs} R_2$$

$$(B3, g) \quad V_o = -g_{fm} V_{in} R_2$$

$$\therefore A_v = -g_{fm} R_2$$

$$\text{Now, } g_{fm} = \frac{\partial I_D}{\partial V_{DS}}$$


$$\therefore g_{fm} = \frac{2.8 + 0.2 I_D}{V_{DS}} = \frac{2 \times 0.1 \text{ mS}}{0.25}$$

$$\therefore g_{fm} = 0.8 \text{ mS}$$

$$A_v = -37.1$$

where minus signs indicate a phase shift of 180° .

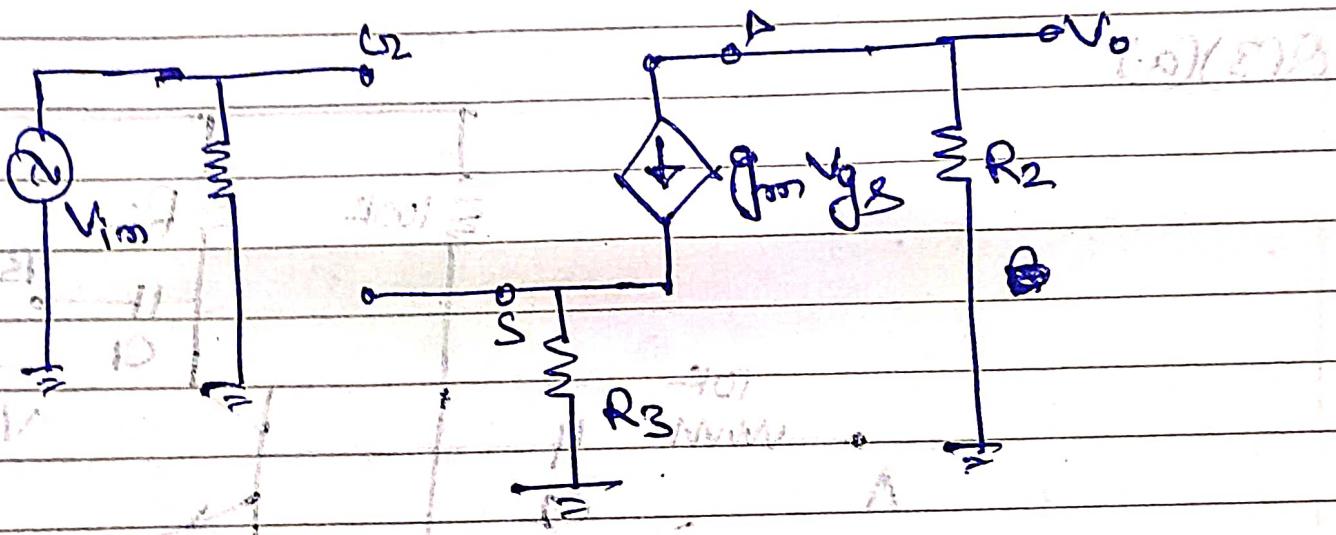Q.2(c) If node C is left open then R_{V3} will also come in picture



$$V_o = -g_{fm} V_{gs} R_2$$

$$V_g = V_{in} \quad ; \quad V_s = R_3 \cdot g_{fm} V_{gs}$$

$$V_{gs} = V_g - V_s = V_{in} - R_3 g_{fm} V_{gs}$$

$$\therefore V_{o/s}(1 + g_m R_3) = V_{in}$$

$$\therefore V_o = \frac{-g_m R_2 V_{in}}{1 + g_m R_3}$$


$$\therefore A_v = \frac{-g_m R_2}{1 + g_m R_3} \quad \textcircled{1}$$

\therefore from $\textcircled{1}$ we see that


if node C is left open R_3 will not be bypassed and hence,

overall gain will reduce by a factor of $(1 + g_m R_3)$.

Q(3)(a.)

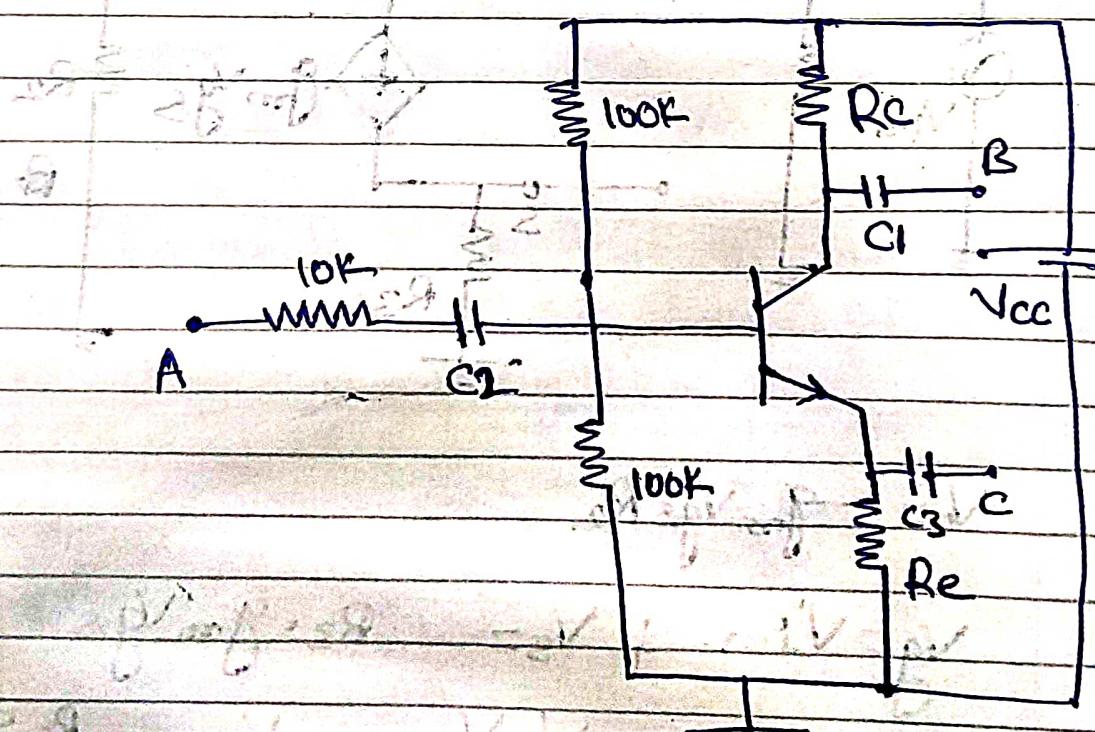

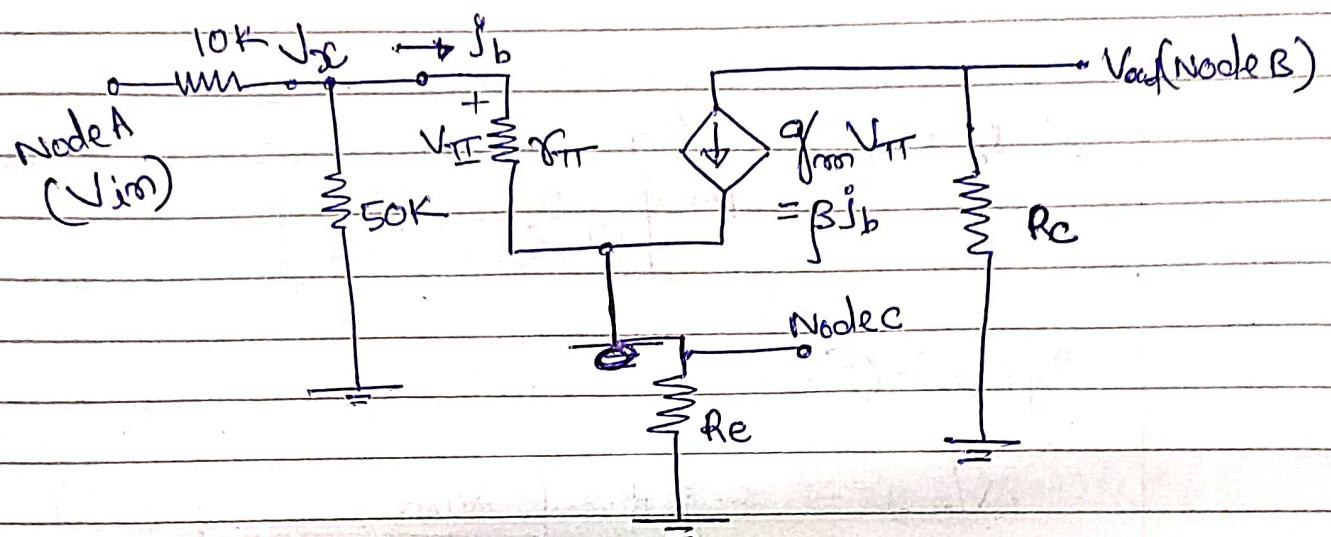Drawing small signal model (neglecting r_o).



For part a : Node C is grounded.

∴ R_E will be bypassed by C_3 for AC signals.

Now, Voltage gain = $\frac{V_{out}}{V_{im}}$

$$V_{out} = -\beta j_b R_C \quad (1)$$

$$\frac{V_{im} - V_x}{10k} = \frac{V_x}{50k} + j_b$$

$$\frac{V_x - 0}{j_T} = j_b \Rightarrow V_x = +j_T j_b$$

$$\frac{V_{im} - j_T j_b}{10k} = \frac{-j_T j_b}{50k} + j_b$$

$$\frac{V_{im}}{10k} = \left[1 + \frac{j_T}{50k} + \frac{j_T}{10k} \right] j_b$$

$$\therefore i_b = \frac{V_{in}}{10K \left[1 + \frac{\gamma_{\pi}}{50K} + \frac{\gamma_{\pi}}{10K} \right]} \quad \textcircled{2}$$

By $\textcircled{1} + \textcircled{2}$

$$V_{out} = -\beta R_C \cdot \left[\frac{V_{in}}{10K \left(1 + \frac{\gamma_{\pi}}{50K} + \frac{\gamma_{\pi}}{10K} \right)} \right]$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{-\beta R_C}{P} = A_{VS}$$

$$\text{where}, P = 10K \left(1 + \frac{\gamma_{\pi}}{50K} + \frac{\gamma_{\pi}}{10K} \right)$$

$$\text{Now, } \gamma_{\pi} = \frac{V_T}{I_B} = \beta \left(\frac{V_T}{I_C} \right)$$

and as per question, γ_{π} will be constant for a given bias point.

| | | |
|------------------|---------|-----------|
| $[A_{VS}]_{max}$ | $= 150$ | $= 3.$ |
| $[A_{VS}]_{min}$ | $= 50$ | \approx |

(b) Here, node C is open, hence R_e will be taken into consideration while gain calculation.

$$\therefore V_{out} = -\beta i_b R_c$$

Applying KCL at node x

$$\frac{V_{in} - V_x}{10k} = \frac{V_x}{50k} + i_b \quad \text{--- (1)}$$

$$\therefore V_x = [\gamma_{\pi} + (\beta+1)R_e] i_b \quad \text{--- (2)}$$

by (1) & (2)

$$A_{vS} = \frac{V_{out}}{V_{in}} = \frac{-R_c}{1 + \frac{\gamma_{\pi} + (\beta+1)R_e}{50k} + \frac{\gamma_{\pi} + (\beta+1)R_e}{10k}}$$

$$\therefore A_{vS} = \frac{-R_c}{1 + \left(\frac{\gamma_{\pi} + (\beta+1)R_e}{50k} \right) G}$$

$$= \frac{-R_c}{\frac{1}{\beta} + \left[\frac{1}{g_m} + R_e \right] \frac{G}{50k}} \quad \left\{ \beta+1 \approx \beta \right\}$$

\therefore At the given bias point

$$g_m = \frac{i_c}{V_T} = 19.3 \text{ A/V}$$

Date: / /

Also, for β_{\max} , A_{VS} will be max.

$$\frac{[A_{VS}]_{\max}}{[A_{VS}]_{\min}} = \frac{\frac{-R_C}{\frac{1}{150} + [19.3 + R_E] \cdot \frac{6}{50k}}}{\frac{-R_C}{\frac{1}{50} + [19.3 + R_E] \cdot \frac{6}{50k}}}$$

$$\frac{(A_{VS})_{\max}}{(A_{VS})_{\min}} = \frac{\frac{1}{50} + (19.3 + R_E) \cdot \frac{6}{50k}}{\frac{1}{150} + (19.3 + R_E) \cdot \frac{6}{50k}} = 1.5$$

$$\therefore R_E = 166.68 \Omega$$