
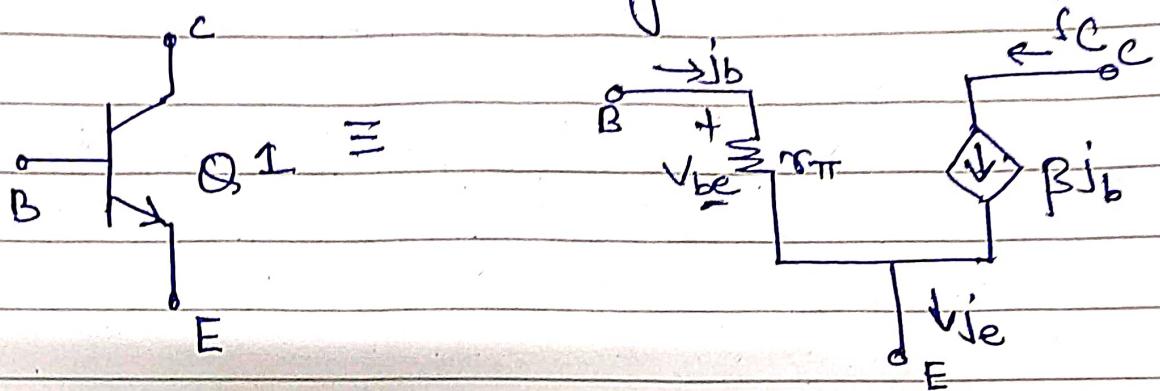


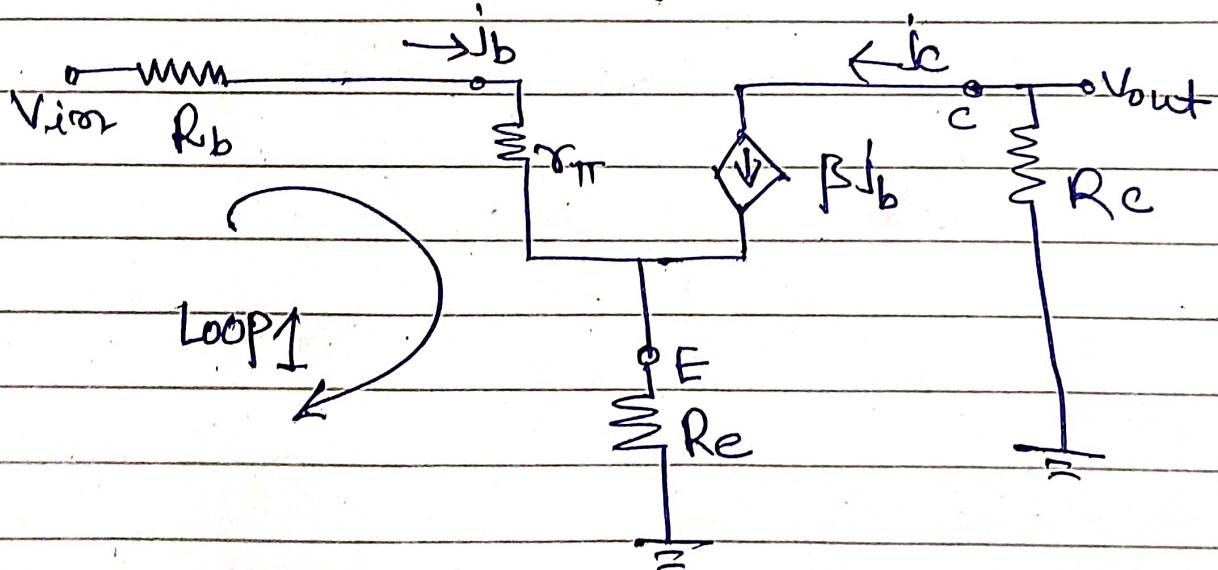Q1. a) Both the circuit given in fig 1 and fig 2 can be converted into small signal AC equivalent circuit for gain calculation.



∴ Analysing the circuit in fig 1



$$V_{out} = -i_c R_C = -\beta j_b R_C \quad \text{--- (1)}$$

For loop 1 applying KVL

$$-V_{im} + R_b i_b + i_b g_{TT} + (1+\beta) i_b R_e = 0$$

$$\therefore \beta = g_m \cdot g_{TT} \Rightarrow g_{TT} = \frac{\beta}{g_m}$$

$$V_{irr} = \left[ R_b + \frac{\beta}{g_m} + (1+\beta) R_e \right] i_b \quad \text{--- (2)}$$

∴ by (1) & (2)

Voltage gain


$$A_v = \frac{V_{out}}{V_{im}} = \frac{-\beta R_c}{R_b + \frac{\beta}{g_m} + (1+\beta) R_e}$$

$$A_v = \frac{-R_c}{\frac{1}{g_m} + \frac{R_b}{\beta} + \frac{1+\beta}{\beta} R_e}$$

∴  $\beta$  is large  $\Rightarrow \beta+1 \approx \beta$


$$A_v \approx \frac{-R_c}{\frac{1}{g_m} + R_e + \frac{R_b}{\beta+1}}$$

Now analysing the circuit in Fig 2:

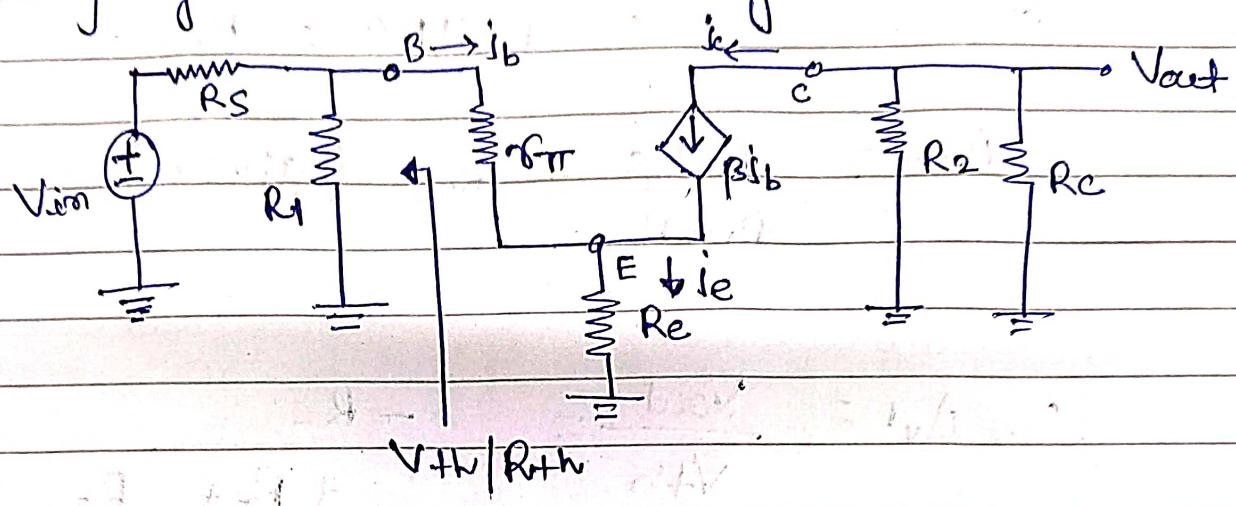

$$V_{th} = \frac{R_1}{R_1 + R_S} \cdot V_{in}, \quad R_{th} = R_1 || R_S$$

The Thevenin eq. ckt will look like

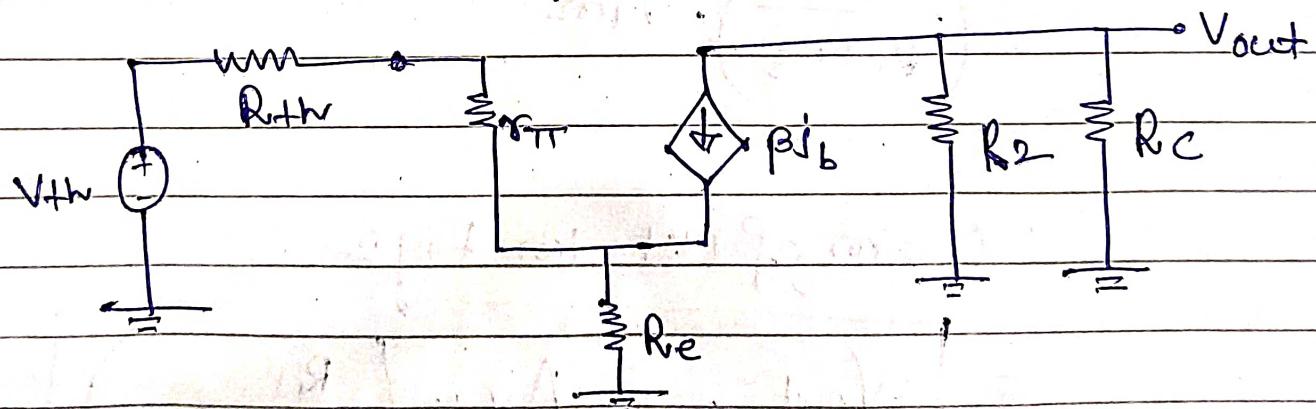

As per the previous analysis of Fig 1 gain of the above ckt can be given as

$$A_v = \frac{V_{out}}{V_{th}} = -\frac{R_C || R_2}{\frac{1}{g_m} + R_E + \frac{R_{th}}{\beta + 1}}$$

given that

$$R_2 \gg R_C$$

$$\therefore R_2 // R_C = R_C$$

$$R_{th} = \frac{R_i \cdot R_s}{R_i + R_s} = R_b \quad (\text{given})$$

$$\therefore A_v^1 = \frac{V_{out}}{V_{th}} = \frac{-R_C}{\frac{1}{g_m} + R_{et} \cdot R_b} = A_v$$

$$\therefore \frac{V_{out}}{\left( \frac{R_i}{R_i + R_s} \right) \cdot V_{in}} = A_v \cdot \frac{R_i}{R_i + R_s}$$

$\therefore$  Gain of CKT in Fig 2

$$= \boxed{\frac{V_{out}}{V_{in}} = A_v \cdot \left( \frac{R_i}{R_i + R_s} \right)}$$

Q.1.(b) Circuit equation obtained in Fig 2 is

$$\frac{V_{out}}{V_{in}} = \frac{-R_C}{\frac{1}{f_m} + R_E + \frac{R_B}{\beta + 1}} \cdot \left( \frac{R_I}{R_I + R_S} \right)$$

From the above equation, the effect of  $\beta$  can be nullified if the  ~~$R_B$~~  term

$\frac{R_B}{\beta + 1}$  can be made negligible in

comparison with the other terms in denominator.

Case 1:  $\rightarrow$  Let us say  $R_B$  is very small, however this is not a practical solution, as  $R_B$  is modeling input source impedance and it will always pose a significant non-zero value.

Case 2:  $\rightarrow$  Very large  $\beta$  ! It has other consequences, Too high beta will vary the operating point ~~too~~ very significantly for a small change in  $I_b$  and the output will be very sensitive to temperature variations.

Case 3:  $\rightarrow Y_{gm}$  factor very high!  $\rightarrow$

This is also not a very practical sol<sup>n</sup> w.r.t the given ckt, as we know

$$g_{fm} = \frac{I_C}{V_T}$$


$V_T$  is constant at a fixed temp.  
(say ambient temperature) and hence,  
we can not make  $I_C$  too small,  
forcing a very small  $I_C$  bias will  
make BJT go into non-linear region  
too often.

Case 4:  $\rightarrow R_E$  very large:


with a suitable biasing arrangement  
we can choose a large  $R_E$ .

However, large  $R_E$  will result in  
a very significant decrease in  
gain. Hence there is a trade off,  
and we need to select an optimum  
value.

Aus 2 a)

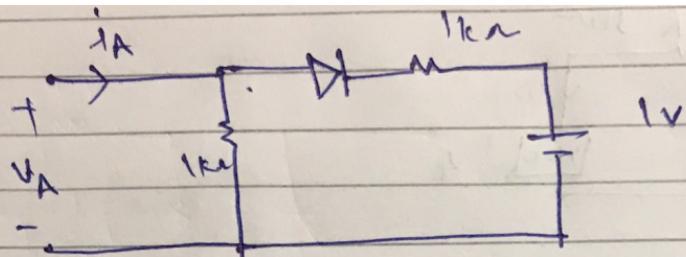

Diode ON  $\oplus$  for  $v_A > 1V$

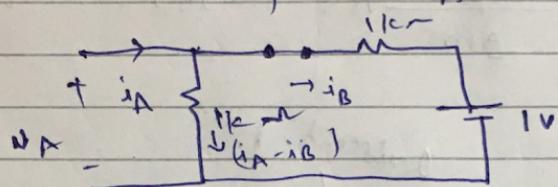

$$v_A = (i_A - i_B) 1k \rightarrow i_B = i_A - v_A - i$$

$$-1 - i_B + v_A = 0$$


$$\Rightarrow v_A = 1 + i_B - i$$

$$\Rightarrow v_A = 1 + i_A - v_A$$

$$\Rightarrow 2v_A = 1 + i_A \Rightarrow i_A = 2v_A - 1 - i$$


$$\Rightarrow v_A = \frac{1+i_A}{2} = 0.5 + 0.5i_A \Rightarrow i_A = 2v_A +$$

Diode OFF for  $v_A < 1V$

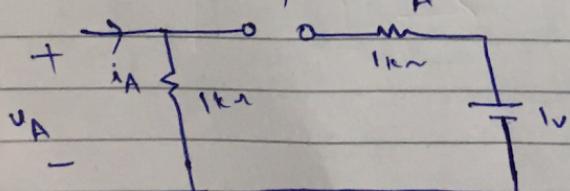


$$v_A = i_A$$

$$\Rightarrow i_A = v_A$$

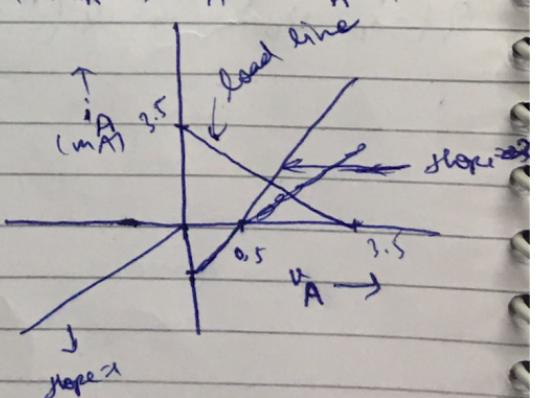

A82 b)

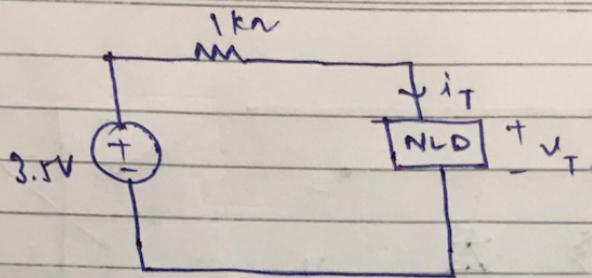

$$-3.5 + i_T + v_T = 0$$

$$\Rightarrow i_T = (3.5 - v_T) \text{ mA}$$

From the figure,  $v_T = v_A$ ,  $i_T = i_A$


$$3.5 - v_A = 2v_A - 1$$

$$\Rightarrow 3v_A = 4.5$$

$$v_A = 1.5V = v_T$$

$$i_T = 3.5 - 1.5$$

$$i_T = 2 \text{ mA}$$

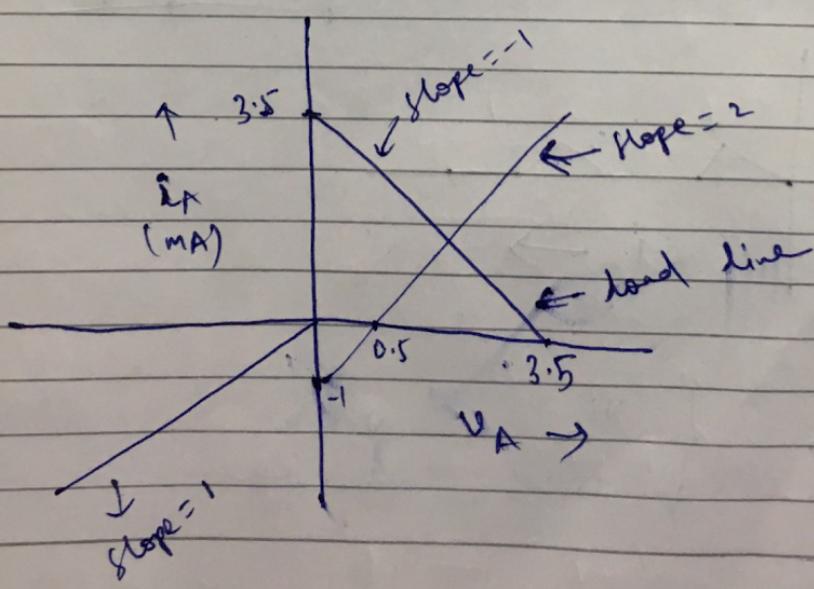

$$Q.3 \text{ a)} \quad V_B = 0.7 \text{ V}$$

Since, the MOSFET (M) drain and gate are shorted, it will always be in saturation.

$$\therefore I_D = \frac{1}{2} \cdot \mu_m C_{ox} \cdot \left( \frac{W}{L} \right) \cdot (V_{ns} - V_T)^2$$

$$\textcircled{a} \quad g_m = \frac{\partial I_D}{\partial V_{ns}} = \frac{1}{2} (\mu_m C_{ox}) \cdot \left( \frac{W}{L} \right) \cdot 2 \cdot (V_{ns} - V_T)$$

$$\therefore V_n = V_B \therefore V_{ns} = V_{BS} = V_B - V_s = 0.7 \text{ V}$$

$$\therefore g_m = \frac{1}{2} \times 100(\mu\text{A/V}) \cdot 10 \cdot 2 \cdot (0.7 - 0.2)$$

$$\therefore g_m = 10^3 \times 10^{-6} \times 0.5 = 0.5 \times 10^{-3}$$

$$\boxed{g_m = 0.5 \frac{\text{mA}}{\text{V}}}$$

$$Q.3 \text{ b)} \quad \text{Here, } V_o = V_B$$

$$\therefore \text{small signal resistance } (r_o) \\ = \frac{\partial V_o}{\partial I_D} = \frac{\partial V_B}{\partial I_D}$$

Since, MOSFET is in saturation

$$I_D = \frac{1}{2} \mu_m C_{ox} \left( \frac{W}{L} \right) (V_{DS} - V_T)^2$$

$$V_D = V_B = V_{DS}$$

$$\therefore I_D = \frac{1}{2} \mu_m C_{ox} \left( \frac{W}{L} \right) (V_B - V_T)^2$$

$$(V_B - V_T) = \sqrt{\frac{2 \cdot I_D}{\mu_m C_{ox} (W/L)}}$$

$$V_B = \sqrt{\frac{2 I_D}{\mu_m C_{ox} (W/L)}} + V_T$$

$$\therefore \frac{\partial V_B}{\partial I_D} = \frac{2}{\sqrt{\frac{2 I_D}{\mu_m C_{ox} (W/L)}}} \cdot \frac{2}{\mu_m C_{ox} (W/L)}$$

$$= \frac{1}{\sqrt{2 I_D \mu_m C_{ox} (W/L)}}$$

$$r_0 = \frac{1}{\sqrt{2 \times I_D \times 100 \times 10^{-6} \times 10}}$$

$$\therefore I_D = \frac{1}{2} \times 100 \times 10^{-6} \times 10 (0.5)^2 = 0.125 \text{ mA}$$


$$r_0 = \frac{1}{[2 \times 0.125 \times 10^{-3} \times 100 \times 10^{-6} \times 10] V_2}$$

$$= \frac{1}{[2 \times 12.5 \times 10^{-8}] V_2} = \frac{1}{5 \times 10^{-4}}$$

$$\therefore r_0 = 0.2 \times 10^4 \Rightarrow r_0 = 2 \text{ k}\Omega$$

Q. 3) c)

M1 is operating in saturation region

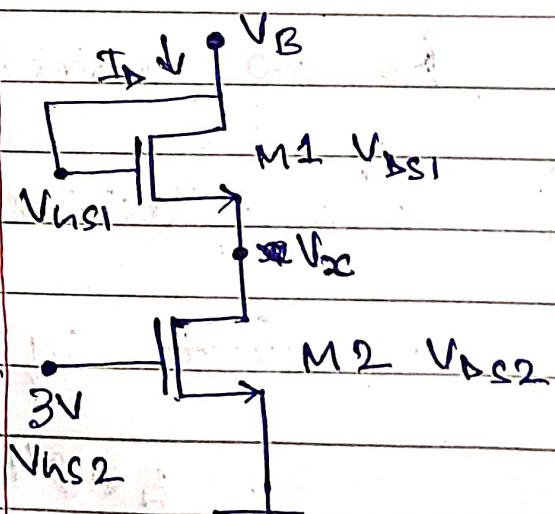

$$\therefore I_D1 = \frac{1}{2} U_m C_{ox} \cdot \frac{W}{L} (V_{GS1} - V_T)^2$$

$$I_D1 = \frac{1}{2} \times 100 \times 10^{-6} \times 10 (V_B - V_{DS1} - 0.2)^2$$

$$I_D1 = 5 \times 10^{-4} (V_B - V_{DS1} - 0.2)^2$$

(1)

Now for M<sub>2</sub> to operate in saturation region

$$V_{DS2} \geq V_{GS2} - V_T \geq (3 - 0.2) \geq 2.8$$

$$\therefore V_{DS2} = V_D \geq 2.8 \text{ V} \quad \textcircled{2}$$

Now, if M<sub>2</sub> will operate in saturation then,

$$I_{D2} = \frac{1}{2} \cdot C_{mox} \cdot \frac{W}{L} (V_{GS} - V_T)^2$$

$$= \frac{1}{2} \cdot 100 \times 10^{-6} \times 10 \times (2.8)^2$$

$$\therefore I_{D2} = 3.92 \times 10^{-3} \text{ A}$$

As no current will go in gate

$$I_D = I_{D2}$$

From eqn ①

$$5 \times 10^{-4} (V_B - V_D - 0.2)^2 = 3.92 \times 10^{-3}$$

$$(V_B - V_{ce} - 0.2)^2 = 0.784 \times 10^1 = 7.84$$

$$V_B - V_{ce} - 0.2 = 2.8$$

$$V_B - 0.2 - 2.8 = V_{ce}$$

$$\text{or, } V_{ce} = V_B - 3$$

For M2 to operate in saturation

$$V_{ce} \geq 2.8V \quad (\text{by } \textcircled{2})$$

$$V_B - 3 \geq 2.8V$$

$$\therefore V_B \geq 5.8V$$

$$V_{B_{\min}} = 5.8V$$

Q.4.2)

$$V_{ov} = 0.3V, I_D = 0.3mA$$

~~$$V_{ov} = V_{SD} - |V_T| = 0.3$$~~

$$V_{SN} = 0.3 + |V_T| = 0.3 + 0.8 = 1.1V$$

$$\therefore V_{sh} = 1.1V$$


$$\therefore V_S = 1.1V$$

$$\therefore I_D = 2.5 - 1.1$$

$R_s$

$$1.4 = 0.3 \text{ mA}$$

$R_s$

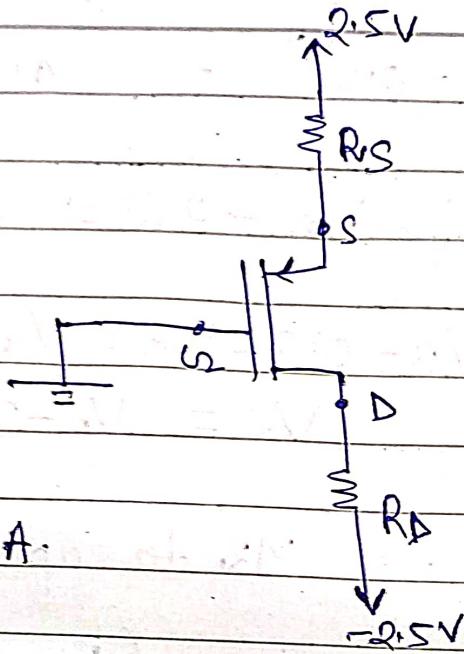

Eq. ckt for DC analysis

$$R_s = \frac{1.4}{0.3} \times 10^3 = 4.67 \text{ K ohm}$$

(Q4)b)

Overall voltage gain ( $G_{ov}$ ) =  $-10(V/V)$

Since, overall voltage gain for the given  
ckt will be:

$= -g_m R_D \rightarrow$  This can be derived  
from small signal model.

$$g_m = \frac{2I_D}{V_{ov}} = \frac{2 \times 0.3}{0.3} = 2 \text{ mA/V}$$

$$\therefore 10 = 2 \cdot R_D \Rightarrow \boxed{R_D = 5 \text{ kN}} \quad \underline{\text{Ans.}}$$