

QUIZ -01

Date: 14-02-2025

INTEGRATED ELECTRONICS

ECE 214

Time 1 Hr. 20 Min.

Max. Marks 20

(All plagiarism policy of IIT Delhi is applicable)

1. For each of the cases mentioned in Table I and Table II find whether the transistor is in active, saturation and cut off mode? (All values are in volts)

Table I for NPN

Case	V_B	V_E	V_C
1.	0.7	0	0.7
2.	0.8	0	0.1
3.	0	-0.7	-0.6
4.	-2.0	-2.7	0

Table II for PNP

Case	V_B	V_E	V_C
1.	-0.68	0	-0.68
2.	-0.78	0	-0.1
3.	0	0.68	0.56
4.	3.18	2.58	0

(4 Marks, CO1, CO2)

2. (a) A npn transistor having a reverse saturation current $I_{CBO} = 10\mu A$ is operated in CE mode. If the base current is $250\mu A$. Calculate I_C and I_E , assume that $\alpha = 0.98$.

(2 Marks, CO2)

- (b) Determine the output waveform for the network of Fig.1 and calculate the average and rms voltage level. (Assuming all diodes are ideal)

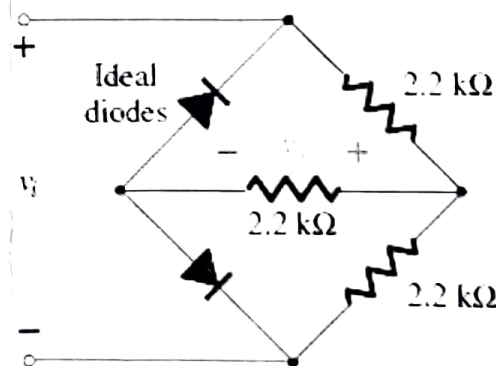
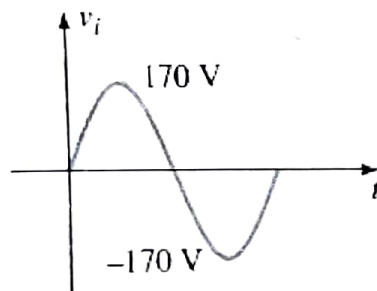


Fig.1

$$I_C = I_B + (\beta + 1) I_{CBO}$$

$$I_C = 12.75 \text{ mA}$$

(3 Marks, CO1, CO2)

3. Given the device characteristics of Fig.2 and Fig.3 for the fixed-bias configuration, considering $V_{BE} = 0.7 \text{ V}$ determine V_{CC} , R_B and R_C .

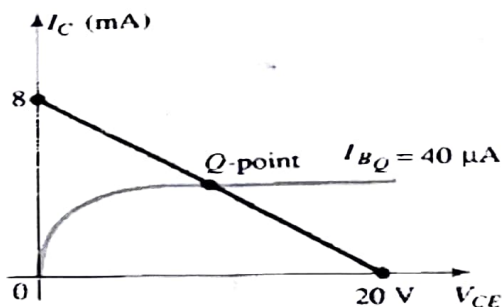


Fig.2

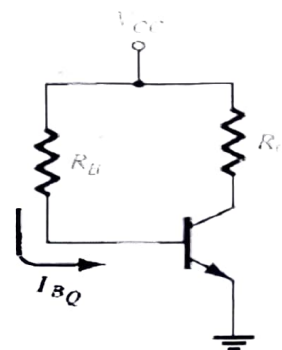


Fig.3

(3 Marks, CO2)

4. From Fig. 4 determine the voltages at all nodes and the currents through all branches. Assume that the transistor β is specified to be at least 50. Considering $V_{BE} = 0.7 \text{ V}$ and also check the BJT is in active mode, if not in active mode, then assume given transistor is in deep saturation mode. Also calculate β_{forced} if required.

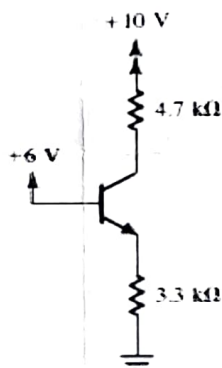


Fig.4

(5 Marks, CO2)

5. Find the values of I and V in the circuits shown in Fig. 5 assume all diodes are ideal.

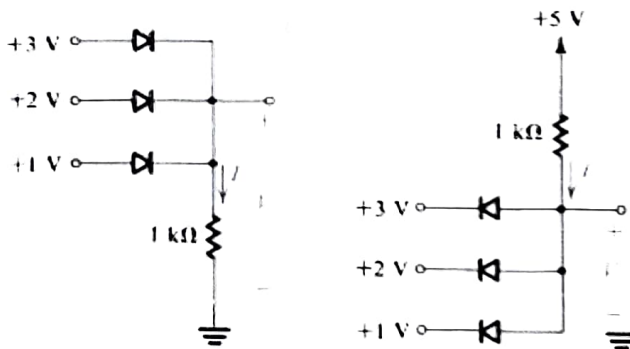


Fig.5

(3 Marks, CO1)

1. For the circuit shown below in fig.1 & fig.2.

- Calculate the o/p voltages V_{o1} and V_{o2} in fig.1(a) and fig.1(b) for $V_m = 4.2V, 5V, 5.7V, 10V$ theoretically.
- When o/p voltage of fig1(a) feeds to input of fig1(b), the cascaded circuit is achieved, shown in fig.2. then calculate o/p voltage of cascaded circuit V_{o2} for $V_m = 4.2V, 5V, 5.7V, 10V$ theoretically.
- Sketch the o/p voltage waveform of the cascaded circuit given in fig.2 for $V_m = 4.2, 5V, 5.7V, 10V$ on LTspice.

Assuming Zener diode as ideal and forward bias voltage drop of normal diode to be $0.7V$
 (Assume $V_i = V_m \sin \omega t$).

+ 5.7
 - same

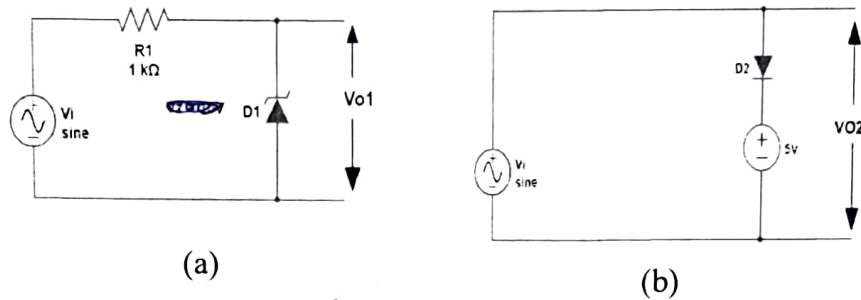


fig.1


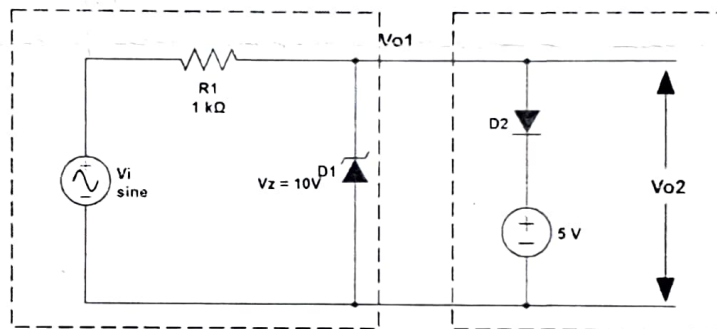


fig.2

Simulation Tutorial 02

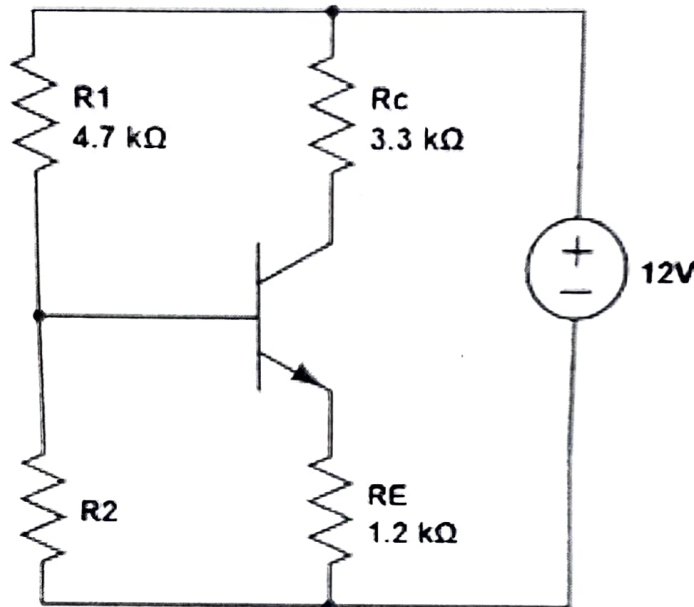1. In the BJT amplifier circuit shown below in Fig.1. Assume V_{BE} is 0.7 V. The collector voltage V_c is given as 5V.
- Draw the Thevenin equivalent of the given circuit and calculate the value of resistance R_2 theoretically, when β is 100. [3 Marks, CO2]
 - Calculate the Q point for $\beta_1=100$ and $\beta_2=150$. (Put R_2 obtained from part(a)) [2 Marks, CO2]
 - Show the operating points and plot the I_c v/s V_{CE} characteristics of Thevenin equivalent circuit when $\beta_1=100$ and $\beta_2=150$ using LTspice. [5 Marks, CO2]

Note: Use transistor 2N2222, NXP, NPN from the library and edit β_1 , and β_2 values according to the question.



$$1396.3 \Omega$$
$$3.56 V$$

$$3.29 V$$
$$3.56 V$$

$$1.29$$

Fig.1